

프로그래밍의 원리 2012 가을 - 실습 5

인터페이스로 프로그래밍해보기, 회로의 확장

서울대학교 프로그래밍 연구실

강동욱, 최민아

2012년 10월 18일

이번 실습의 목적은:

- 지난 숙제의 상태가 없는 회로문제(combinational circuit)를 스위치와 상태가 있는 회로(sequential circuit)로 확장하여, 명령형(imperative) 프로그래밍과 값중심(applicative) 프로그래밍의 차이를 익혀봅니다.


연습문제

명령형 관련 교수님 슬라이드 참고하세요 (링크를 최근 강의록으로 수정하였습니다.)

<http://ropas.snu.ac.kr/~kwang/4190.210/12/3.pdf>

 1. 상태가 있는 회로(sequential circuit)

지난 숙제2에서 만들었던 회로(circuit)는 전기가 한번 흐르고 나면 출력이 하나로 정해집니다. 이런 회로를 상태가 없는 회로(combinational circuit)라고 합니다. 이런 상태가 없는 회로들을 서로가 서로를 맞물리게 연결할 수 있습니다. 그러면 시간에 따라서 전깃줄(wire)의 상태가 계속 변하는 상태 있는 회로(sequential circuit)가 됩니다. 예를 들어 다음과 같이 NOT 게이트(gate) 세개를 연결하면 각 전깃줄의 전위(voltage)가 0과 1로 반복적으로 변하게 되지요.



우리는 이번 실습에서 이와같이 게이트의 출력이 다시 입력으로 들어갈 수 있는 회로를 구성할 것입니다. 여기에 더해서 기존과 같이 입력값을 고정하지 않고 사용자가 0과 1을 켜고 끌 수 있는 스위치를 추가 합니다.

(각 게이트의 신호전달시간(propagation time)은 동일하다고 가정. 단위시간이 지날 때마다 게이트의 입력이 출력으로 변하여 나옵니다.)

아래의 함수들을 값중심으로 만드십시오.

(a) 회로를 만들고 사용하는 함수:

```
empty-circuit : circuit
add-gate-to-circuit : gate-name * gate * circuit → circuit
and-gate : wire * wire * wire → gate
or-gate : wire * wire * wire → gate
not-gate : wire * wire → gate
switch : wire → gate
match-gate : wire * circuit → gate
input-wire : gate * nat → wire
output-wire : gate → wire
is-and? : gate → bool
is-or? : gate → bool
is-not? : gate → bool
is-switch? : gate → bool
```

match-gate는 전깃줄과 회로를 받아 인자로 넘겨준 전깃줄이 출력(output wire)인 게이트를 찾아줍니다.

(b) 회로 상태를 만들고 사용하는 함수들:

```
set-wire-volts : initial-wire-volts * circuit → circuit × state
one : volt
zero : volt
step : circuit × state → circuit × state
run : circuit × state * nat → circuit × state
print : circuit × state → void
```

프린트 방법은 전깃줄 이름 전위 형식으로 써주세요 예를들어

```
w1 0
w2 1
...
```

*참고

initial-wire-volt = (*wire* × *volt*) list

wire = string

switch = string

gate-name = string

아래의 함수들을 구현하세요. 전깃줄(wire)에 대해 명령형으로 만드십시오.

(a) 회로를 만들고 사용하는 함수:

```
empty-circuit : circuit
add-gate-to-circuit : gate-name * gate * circuit → circuit
    one : volt
    zero : volt
make-wire : name → wire
set-wire : wire * volt → wire
volt-wire : wire → volt
and-gate : wire * wire * wire → gate
or-gate : wire * wire * wire → gate
not-gate : wire * wire → gate
switch : wire → gate
match-gate : wire * circuit → gate
input-wire : gate * nat → wire
output-wire : gate → wire
is-and? : gate → bool
is-or? : gate → bool
is-not? : gate → bool
is-switch? : gate → bool
```


(b) 회로 상태를 만들고 사용하는 함수들:

```
set-wire-volts : initial-wire-volts * circuit → circuit
step : circuit → circuit
run : circuit * nat → circuit
print : circuit → void
```

 2. 안정된 회로(collecting wire states)

어떤 회로에서 전깃줄이 가질 수 있는 전위들을 알아보고 싶습니다. 즉 어떤 전깃줄이 동작 중에 스위치에 상관 없이 항상 0만 가지는지 혹은 항상 1만 가지는지, 0과 1을 다 가질 수 있는지 체크해보고 싶습니다. 회로 상태에서 스위치 입력은 무시했을때 각 전깃줄마다 저장될수 있는 전위(volt) 집합을 구해보십시오. 값중심 프로그래밍으로만 만들어 봅니다.

```
collect : circuit * initial-wire-volts → (wire × (volt list)) list
```



```

(define and1 (and-gate "w1" "w2" "w3"))
(define or1 (or-gate "w3" "w4" "w5"))
(define not1 (not-gate "w5" "w2"))
(define switch1 (switch "w1"))
(define switch2 (switch "w4"))
(define circuit1 (add-gate-to-circuit "and1" and1 empty-circuit))
(define circuit2 (add-gate-to-circuit "or1" or1 circuit1))
(define circuit3 (add-gate-to-circuit "not1" not1 circuit2))
(define circuit4 (add-gate-to-circuit "switch1" switch1 circuit3))
(define circuit5 (add-gate-to-circuit "switch2" switch2 circuit4))
(define circuit-state
  (set-wire-volts
    (list
      (cons "w1" zero) (cons "w2" zero)
      (cons "w3" zero) (cons "w4" one) (cons "w5" one))
    circuit5))
(print (run circuit-state 1))
> w1 0
> w2 0
> w3 0
> w4 1
> w5 1

(collect circuit5
  (list
    (cons "w1" zero) (cons "w2" zero)


```

```

      (cons "w3" zero) (cons "w4" one) (cons "w5" one)))

(define w1 (make-wire "w1"))
(define w2 (make-wire "w2"))
(define w3 (make-wire "w3"))
(define w4 (make-wire "w4"))
(define w5 (make-wire "w5"))
(define and1 (and-gate w1 w2 w3))
(define or1 (or-gate w3 w4 w5))
(define not1 (not-gate w5 w2))
(define switch1 (switch w1))
(define switch2 (switch w4))
(define circuit1 (add-gate-to-circuit "and1" and1 empty-circuit))
(define circuit2 (add-gate-to-circuit "or1" or1 circuit1))
(define circuit3 (add-gate-to-circuit "not1" not1 circuit2))
(define circuit4 (add-gate-to-circuit "switch1" switch1 circuit3))
(define circuit5 (add-gate-to-circuit "switch2" switch2 circuit4))
(define circuit-state
  (set-wire-volts
   (list
    (cons w1 zero) (cons w2 zero)
    (cons w3 zero) (cons w4 one) (cons w5 one))
   circuit5))
(print (run circuit-state 1))
> w1 0
> w2 0
> w3 0
> w4 1
> w5 1

```

 

```


(define and1 (and-gate "w1" "w2" "w3"))
(define not1 (not-gate "w3" "w1"))
(define switch1 (switch "w2"))
(define circuit1 (add-gate-to-circuit "and1" and1 empty-circuit))
(define circuit2 (add-gate-to-circuit "not1" not1 circuit1))
(define circuit3 (add-gate-to-circuit "switch1" switch1 circuit2))
(define circuit-state
  (set-wire-volts
    (list (cons "w1" one) (cons "w2" one) (cons "w3" zero)) circuit3))
(print (run circuit-state 3))
> w1 0
> w2 1
> w3 0
(collect circuit3 (list (cons "w1" one) (cons "w2" one) (cons "w3" zero)))

```

```

(define w1 (make-wire "w1"))
(define w2 (make-wire "w2"))
(define w3 (make-wire "w3"))
(define and1 (and-gate w1 w2 w3))
(define not1 (not-gate w3 w1))
(define switch1 (switch w2))
(define circuit1 (add-gate-to-circuit "and1" and1 empty-circuit))
(define circuit2 (add-gate-to-circuit "not1" not1 circuit1))
(define circuit3 (add-gate-to-circuit "switch1" switch1 circuit2))
(define circuit-state
  (set-wire-volts
    (list (cons w1 one) (cons w2 one) (cons w3 zero))
    circuit3))
(print (run circuit-state 3))
> w1 0
> w2 1
> w3 0

```

 

```

(define or1 (or-gate "w1" "w2" "w3"))
(define not1 (not-gate "w3" "w1"))
(define switch1 (switch "w2"))
(define circuit1 (add-gate-to-circuit "or1" or1 empty-circuit))
(define circuit2 (add-gate-to-circuit "not1" not1 circuit1))
(define circuit3 (add-gate-to-circuit "switch1" switch1 circuit2))
(define circuit-state
  (set-wire-volts
    (list
      (cons "w1" zero) (cons "w2" zero) (cons "w3" one))
    circuit3))
(print (run circuit-state 3))
> w1 1
> w2 0
> w3 1
(collect circuit3 (list (cons "w1" zero) (cons "w2" zero) (cons "w3" one)))

(define w1 (make-wire "w1"))
(define w2 (make-wire "w2"))
(define w3 (make-wire "w3"))
(define or1 (or-gate w1 w2 w3))
(define not1 (not-gate w3 w1))
(define switch1 (switch w2))
(define circuit1 (add-gate-to-circuit "or1" or1 empty-circuit))
(define circuit2 (add-gate-to-circuit "not1" not1 circuit1))
(define circuit3 (add-gate-to-circuit "switch1" switch1 circuit2))
(define circuit-state
  (set-wire-volts
    (list (cons w1 zero) (cons w2 zero) (cons w3 one))
    circuit3))


```



```

> w1 1
> w2 0
> w3 1

```

 

```

(define and1 (and-gate "w1" "w2" "w3"))
(define not1 (not-gate "w3" "w4"))
(define not2 (not-gate "w4" "w1"))
(define switch1 (switch "w2"))
(define circuit1 (add-gate-to-circuit "and1" and1 empty-circuit))
(define circuit2 (add-gate-to-circuit "not1" not1 circuit1))
(define circuit3 (add-gate-to-circuit "not2" not2 circuit2))
(define circuit4 (add-gate-to-circuit "switch1" switch1 circuit3))
(define circuit-state
  (set-wire-volts
    (list
      (cons "w1" zero) (cons "w2" zero) (cons "w3" zero) (cons "w4" one))
    circuit4))
(print (run circuit-state 1))
> w1 0
> w2 0
> w3 0
> w4 1
(collect circuit4 (list (cons "w1" zero) (cons "w2" zero) (cons "w3" zero)))

(define w1 (make-wire "w1"))
(define w2 (make-wire "w2"))
(define w3 (make-wire "w3"))
(define w4 (make-wire "w4"))
(define and1 (and-gate w1 w2 w3))

```

```
(define not1 (not-gate w3 w4))
(define not2 (not-gate w4 w1))
(define switch1 (switch w2))
(define circuit1 (add-gate-to-circuit "and1" and1 empty-circuit))
(define circuit2 (add-gate-to-circuit "not1" not1 circuit1))
(define circuit3 (add-gate-to-circuit "not2" not2 circuit2))
(define circuit4 (add-gate-to-circuit "switch1" switch1 circuit3))
(define circuit-state
  (set-wire-volts
    (list
      (cons w1 zero) (cons w2 zero) (cons w3 zero) (cons w4 one))
    circuit4))
(print (run circuit-state 1))
> w1 0
> w2 0
> w3 0
> w4 1
```